



G

O

D

O

O

O

O


D

Filters

single pole:  $\frac{H_0}{1 + \frac{s}{\omega_c}}$




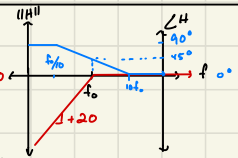inverted pole:  $\frac{1}{1 + \frac{s}{\omega_c}}$



inverted pole = zero + regular pole

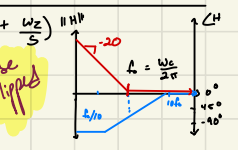
inverted zero:  $(1 + \frac{s}{\omega_c})$




right hand

$1 - \frac{\omega_c}{s}$  phase flipped

regular zero  $(1 + \frac{s}{\omega_c})$

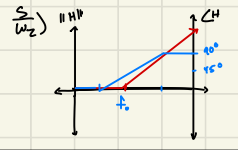


$\frac{\omega}{\omega_c}$

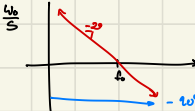

Graphical

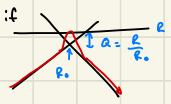- if R crosses L:  $f = \frac{R}{2\pi L}$
- if R crosses C:  $f = \frac{1}{2\pi RC}$
- if L crosses C:  $f = \frac{1}{2\pi \sqrt{LC}}$
- if C crosses axis:  $f = \frac{1}{2\pi RC}$



$R_L = \sqrt{\frac{L}{C}}$   
 $R_L C = Q$

Convolution



$x(t) \rightarrow H(s) \rightarrow y(t)$   
impulse response  
 $H(s) = \int_{-\infty}^{\infty} H(s) e^{st} dt$

$y(t) = \int_{-\infty}^{\infty} h(t-\tau) x(\tau) d\tau$

$h(t) = u(t) - u(t-1)$



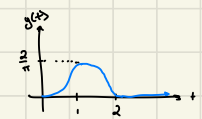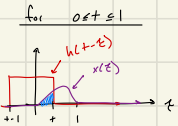
input  $x(t) = \begin{cases} \sin(\pi t), & 0 \leq t \leq 1 \\ 0, & \text{otherwise} \end{cases}$




$y = \int_0^1 \sin(\pi \tau) d\tau$   
 $y = \frac{1}{\pi} (-\cos(\pi \tau))_0^1$   
 $y = \frac{1 - \cos(\pi)}{\pi}$

$y(t) = ?$  for  $0 < t < 1$

for  $1 < t < 2$

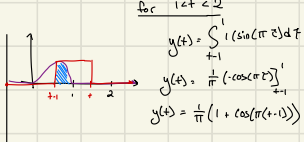

RLC Filter

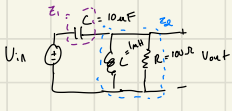

Solved with Algebra

$G(s) = \frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} = \frac{R || sL}{sC + R || sL}$

$\Rightarrow \frac{R sL}{sC + R + sL} = \frac{R s^2 L}{s^2 C L + s(R + L) + R}$

$\Rightarrow \frac{s^2 L}{1 + \frac{s^2 L}{R} + \frac{sL}{R}}$

$\frac{L}{R} = \frac{1}{Q \omega_0}$     $Q = \frac{R}{\omega L}$

plug in #'s  
 $f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi \sqrt{LC}} = 1.6 \text{ kHz}$   
 $Q = (100) \sqrt{\frac{10^{-6}}{10^{-3}}} = 10 = 20 \text{ dB}$

Construct Asymptotes

magnitude: numerator:  $(\frac{s}{\omega_0})^2 = 0dB \rightarrow +20dB/dec$   
denominator:  $\frac{1}{1 + \frac{s}{Q\omega_0} + (\frac{s}{\omega_0})^2} = 0dB \rightarrow -20dB/dec$

putting both together




Phase: numerator:  $(\frac{s}{\omega_0})^2 = +180^\circ$



denominator:  $\frac{1}{1 + \frac{s}{Q\omega_0} + (\frac{s}{\omega_0})^2} = -180^\circ$

combine:

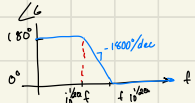

Complex Zero  $1 + \frac{s}{\omega_0} + (\frac{s}{\omega_0})^2$    Complex Pole  $1 + \frac{s}{\omega_0} + (\frac{s}{\omega_0})^2$

As Q increases the slope of the phase gets tighter

When constructing bode plots, since smaller values in parallel & larger in series

$s^2 + 2\zeta\omega_0 s + \omega_0^2 = 1 + 2\zeta \frac{s}{\omega_0} + (\frac{s}{\omega_0})^2 = 1 + \frac{s}{Q\omega_0} + (\frac{s}{\omega_0})^2$     $Q = \frac{1}{2\zeta}$

$\zeta > 1$  real roots (overdamped)    $\zeta = 1$  repeated (critically)    $\zeta < 1$  complex roots (underdamped)

$f = \frac{\omega_0}{2\pi}$     $20 \log(10) = 20$     $20 \log(100) = 40$     $20 \log(1000) = 60$

Combined Construction Note

$\mu = 10^{-6}$     $M = 10^{-3}$     $n = 10^{-9}$

$V_{in} = \frac{R_1}{R_1 + R_2}$     $V_{out} = V_1 \frac{R_2}{R_1 + R_2}$


Impedance parallel  $\frac{Z_1 Z_2}{Z_1 + Z_2}$

common  $\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$

$\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$

slope = -100 dB

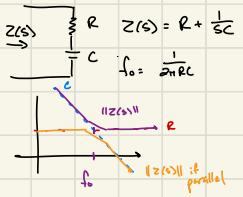$G(s) = \frac{V_{out}}{V_{in}} = \frac{Z_{out}}{Z_1}$



$$G(s) = \frac{R_1}{R_2} \frac{1 + sR_2C}{1 + s\left(\frac{R}{R_1} + R_2C\right) + s^2LC} = G_0 \frac{\left(1 + \frac{s}{\omega_0}\right)}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

$$G_0 = \frac{R_1}{R_2} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad f_0 = \frac{1}{\sqrt{LC}(2\pi)}$$

$$\omega_c = \frac{1}{RC} \quad f = \frac{1}{RC(2\pi)}$$

Improper Rational Function  
 → order num. > order den  
 → use long division

Residues  
 must be proper rational

Simple Poles:  $k_i = (s-p_i)F(s)|_{s=p_i}$   
 Complex Roots: appear in conjugate pairs  
 $k = |k|e^{j\theta} \quad k^* = |k|e^{-j\theta}$   
 $\rightarrow 2|k|e^{j\theta} \left( \frac{e^{j(\theta t + \phi)}}{s - \alpha + j\beta} + \frac{e^{-j(\theta t + \phi)}}{s - \alpha - j\beta} \right)$   
 $\rightarrow 2|k|e^{\alpha t} \cos(\beta t + \phi)$

$\tan^{-1}\left(\frac{\text{Imag}}{\text{Real}}\right)$

Ex: multiple poles  
 $\frac{4(s+3)}{s(s+2)^2}$  or  $k_1 = \frac{3}{5}, k_2 = \frac{1}{5}$   
 $\frac{1}{(s+2)^2} \frac{4(s+3)}{s(s+2)} = \frac{k_1}{s} + \frac{k_2}{s+2}$   
 $k_1 = \lim_{s \rightarrow 0} (sF(s)) = \frac{4(3)}{2} = 6$   
 $k_2 = \lim_{s \rightarrow -2} (s+2)F(s) = \frac{4(-2+3)}{-2} = -2$   
 $\left(\frac{1}{s+2}\right)' \left(\frac{6}{s} - \frac{2}{s+2}\right) \rightarrow \frac{-6}{(s+2)^2} + \frac{2}{(s+2)^2}$   
 $k_1 = \frac{6}{(s+2)^2} + \frac{k_2}{s}$   
 $k_1 = F(s)(s+2) = \frac{6}{s} - 3$   
 $k_2 = \frac{6}{s+2} = 3$   
 $F(s) = \frac{6}{s} - \frac{3}{s+2} + \frac{3}{(s+2)^2}$   
 $(3 - 3e^{-2t} - 2te^{-2t})u(t)$

Laplace Transforms

$F(s) = \int_0^\infty f(t)e^{-st} dt$   
 Time shifted?  
 $\int_0^\infty f(t-a)u(t-a) dt = e^{-as}F(s)$   
 Ex:  $\int_0^\infty \cos(\omega t)u(t-a) dt$   
 $\cos(\omega(t-a) + \phi)u(t-a)$   
 $\cos(\omega(t-a) + \omega a)u(t-a)$   
 apply trig identity  $\rightarrow \cos(\omega a + \phi) = \cos \omega a \cos \phi - \sin \omega a \sin \phi$   
 $\cos(\omega a) e^{-at} \frac{s}{s^2 + \omega^2} + \sin(\omega a) e^{-at} \frac{\omega}{s^2 + \omega^2}$


Laplace Wave form

Laplace of triangular pulse  
  
 $f(t) = (P/a)t(u(t) - u(t-a))$   
 $+ (P/2)(-P/a + 2P)(u(t-a) - u(t-2a))$   
 $f(t)_2 = -P/a(t-a)u(t-a) + P(u(t-a) - u(t-2a))$   
 $\int (f(t)_1 + f(t)_2) = \dots$   
 $F(s) = \frac{P}{a^2s} (1 - 2e^{-as} + e^{-2as})$


If triangular Pulse Periodic

$F(s) = \frac{F_1(s)}{1 - e^{-sT}}$   
 from above  
 $= \frac{P}{a^2s} \frac{(1 - 2e^{-as} + e^{-2as})}{1 - e^{-sT}}$


Transforming Circuits

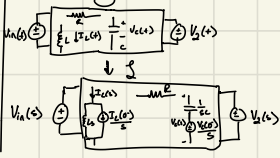

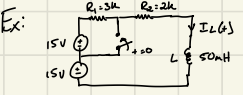Ex:  $V_o(s) = \frac{V_{in}(s)}{1 + sRC}$   
 impulse response of circuit  
 evaluated with all sources not  
 Vals set to 0





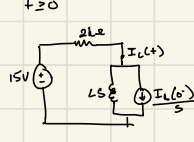Ex:  $I_L(t) = ?$  +20 switch open  
 $V = IR$   
 $I = \frac{V}{R} = \frac{30V}{5000\Omega} = 6mA$   
 $I_L(s) = 6mA$



Ex:  $I_L(t) = ?$   
 use superposition  
 + turn off one all sources but one and do analysis  
 - do this until all sources have been on  
 - it → wire → open  
 - add terms  
 $I_L(s) = \frac{15}{s(2k+1S)} + \frac{I_L(s)}{(2k+1S)} = \frac{15 + (2k)I_L(s)}{s(2k+1S)}$   
 Isolate s terms to s

Thevenin Equivalence

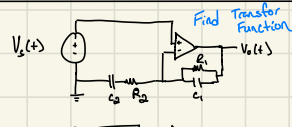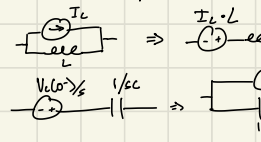

Find Transfer Function  
 $V_o(s)$   
 no  $V_c$  sources  
 always transfer function

2: +1 / 4: → make sure to simplify to 1/2 + 1/4

Laplace Diff Eq

RC diff eq  $V(s) = V_{in}(s)$   
 $V(s) = V_o$   
 $V_{in}(s) \rightarrow A \frac{V_o(s)}{s}$   
 $V(s) = \int V_o(s) dt$   
 $RC(sV_o - V_o) = V_{in}(s)$   
 $V_o(s)(RCs - 1) = \frac{A}{s}(1 - e^{-ts}) + RC V_o$   
 $V_o(s) = \frac{A}{s(RCs - 1)} + RC V_o$

$\frac{15}{s} + 0(I_L(s)) = I_L(s)$   
 $s = \frac{15}{s} + s$   
 $I_L(s) = \int I_L(s) dt$

USE Partial Fraction  
 $I_L(s) = \frac{k_1}{s} + \frac{k_2}{(2k+s)}$   
 $k_1 = \frac{15}{s} \Big|_{s=0} = \frac{15}{2k}$   
 $k_2 = \frac{15}{2k+s} \Big|_{s=-2k} = \frac{15}{-2k} = -\frac{15}{2k}$   
 $I_L(t) = \left( \frac{15}{2k} + \frac{15}{2k} e^{-2kt} \right) u(t)$   
 $I_L(s) = \left( 7mA + 1.5mA e^{-1/500s} \right) u(t)$

Plotting Poles  
 Finding roots. Plot Roots  
 $F(s) = \frac{2s}{(s+2)(s^2+4s+5)}$   
 roots:  $-2$   
 $-2 \pm i$



Fourier Transform of Wave  
 $C_n = \frac{1}{T} \int_0^T v(t) e^{-jn\omega t} dt$   
 $\omega = \frac{2\pi}{T} = \frac{1}{T} \int_0^T v(t) dt$   
 $v(t) = a_0 + \sum_{n=1}^{\infty} b_n \sin(n\omega t) + a_n \cos(n\omega t)$   
 $C_n = \frac{a_n - j b_n}{2}$   
 when  $a_n = 0$   $b_n = 2j C_n$   
 when  $b_n = 0$   $a_n = 2 C_n$

$v_1 \rightarrow G(s) \rightarrow v_2$   
 cutoff = 5 kHz, critically damped second order highpass  
 $C_0 = 20 dB$   
 $G_0 = \frac{1}{1 + \frac{\omega^2}{\omega_c^2} + (\frac{\omega}{\omega_c})^2}$   
 $\omega_0 = 31.4 \text{ kHz}$   
 $C_0 = 10$   
 $\frac{1}{Q} = 2.8$   
 $Q = \frac{1}{2.8}$

$v_1$  is a 500 Hz wave  
 $v_2(t) = \sum_{n=1,3,5,\dots} a_n \cos(n\omega t) + b_n \sin(n\omega t)$   
 $\Rightarrow v_2(t) = \sum_{n=1,3,5,\dots} A_n \cos(n\omega t + \theta_n)$   
 $A_n = \frac{\sqrt{2} V_{pk}}{\sqrt{2}} = b_n$   
 $V_{pk} = 5V$   
 $A_n = \sqrt{a_n^2 + b_n^2} = \frac{V_{pk}}{\sqrt{2}}$   
 $\theta_n = \tan^{-1}(-\frac{b_n}{a_n}) = -45^\circ$

Fourier Series thru transfer function

$V_{out} = \sum_{n=1,3,5,\dots} G_n a_n + A_n \parallel G(jn\omega) \parallel \cos(n\omega t + \theta_n) + G(jn\omega)$

$\parallel G(s) \parallel = \parallel \frac{C_0}{1 + \frac{\omega^2}{\omega_c^2} + (\frac{\omega}{\omega_c})^2} \parallel = \frac{C_0}{\sqrt{1 + (\frac{\omega}{\omega_c})^2 + (\frac{\omega}{\omega_c})^4}}$   
 $\angle G(s) = \tan^{-1}(\frac{\omega}{\omega_c} + \frac{1}{\omega_c^2 \omega})$

$V_{out}(t) = \sum_{n=1,3,5,\dots} \frac{A_n}{\sqrt{2}} \parallel G(s) \parallel \cos(n\omega t - \frac{\pi}{4} - \angle G(s))$

Finding Fourier Coefficients  
 $a_0 = \frac{1}{T} \int_0^T v(t) dt$  (average)  
 $a_n = \frac{2}{T} \int_0^T v(t) \cos(n\omega t) dt$   
 $b_n = \frac{2}{T} \int_0^T v(t) \sin(n\omega t) dt$

$C_n$  purely Real or Imag?  
 zero for even n?  
 odd symmetry  
 $a_n = 0$  purely imaginary  
 no half wave  
 not zero for even n

Magnitude of  $n^{\text{th}}$  harmonic?  
 $n=5$  plug in values + solve

Wave Split into Fourier

Even:  $v(t) = v(-t)$


$a_n = \frac{4}{T} \int_0^{T/2} v(t) \cos(n\omega t) dt$   
 $a_0 = \frac{2}{T} \int_0^{T/2} v(t) dt$   
 $b_n = 0$   
 **$C_n$  only Real**

Odd:  $v(t) = -v(-t)$

$a_n = 0$   
 $a_0 = 0$   
 $b_n = \frac{4}{T} \int_0^{T/2} v(t) \sin(n\omega t) dt$   
 **$C_n$  only Imag**

Half wave: **no DC component**

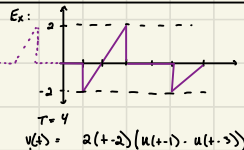$a_n = 0$   
 $a_0 = 0$   
 $b_n = 0$  for  $n = 0, 2, 4, \dots$   
 $a_n = \begin{cases} 0, & \text{even } n \\ \frac{4}{T} \int_0^{T/2} v(t) \cos(n\omega t) dt, & \text{odd } n \end{cases}$   
 $b_n = \begin{cases} 0, & \text{even } n \\ \frac{4}{T} \int_0^{T/2} v(t) \sin(n\omega t) dt, & \text{odd } n \end{cases}$



Ex:  $T = 4$   
 $v(t) = 2(t-2)u(t-1) - 2(t-3)u(t-3)$   
 $v(t) = 2((t-1)-1)u(t-1) - 2((t-3)-1)u(t-3)$   
 $v(t) = 2(t-1)u(t-1) - 2u(t-1) - 2(t-3)u(t-3) + 2u(t-3)$   
 $\int v(t) dt = \frac{2t^2}{2} - \frac{2t^2}{2} - \frac{2(t-3)^2}{2} + \frac{2(t-3)^2}{2}$   
 $= \frac{2t^2}{2} - \frac{2t^2}{2} + \frac{2t^2}{2} - \frac{2t^2}{2}$   
 $v(t) = \frac{v(t)}{1 - e^{-j\omega t}} = \frac{2t^2}{2} (\frac{1}{2} - 1 - \frac{e^{-j\omega t}}{2} - e^{-2j\omega t})$

Fourier  
 $C_n = \frac{1}{T} \int_0^T v(t) e^{-jn\omega t} dt$   
 $\omega = \frac{2\pi}{T} = \frac{\pi}{2}$   
 $C_n = \frac{2e^{-jn\omega t}}{jn\omega T} (\frac{1}{jn\omega} - 1 - \frac{e^{-jn\omega t}}{jn\omega} + e^{-2jn\omega t})$

Forms of Fourier

Rectangular:  $a_0 = \text{average DC value}$   
 $v(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos(n\omega t) + b_n \sin(n\omega t)$   
Polar:  
 $A_n = \sqrt{a_n^2 + b_n^2} = \text{all call } \theta_n = -\tan^{-1}(\frac{b_n}{a_n}) = \angle C_n$   
 $v(t) = a_0 + \sum_{n=1}^{\infty} A_n \cos(n\omega t + \theta_n)$

Second Order Systems

$G(s) = \frac{1}{1 + \frac{s}{\omega_c} + (\frac{s}{\omega_c})^2} = \frac{1}{1 + 2\zeta \frac{s}{\omega_c} + (\frac{s}{\omega_c})^2}$   
 low pass  
 $Q > 1/2 \Rightarrow \zeta < 1$  complex poles  
 $Q < 1/2 \Rightarrow \zeta > 1$  2 Real Poles  
 Critically Damped  
 $\zeta = 1/2$   
 $\omega_c = 2\zeta$   
 $\angle G$  plot showing phase from 0 to -180 degrees.

Butterworth filter

Always Imag  
 3rd order Ex:  $\frac{1}{(1 + \frac{s}{\omega_c})(1 + \frac{s}{\omega_c} + \frac{s^2}{\omega_c^2})}$   
 $Q = \frac{1}{2}$

Chebyshev

Euler: Exponential  
 $v(t) = \sum_{n=-\infty}^{\infty} C_n e^{jn\omega t}$

High pass filter:  $\frac{\omega_c}{s}$   
 Low pass filter:  $\frac{s}{\omega_c}$





$G(s)$  will factor to  $\frac{1}{(1 + \frac{s}{\omega_c})(1 + \frac{s}{\omega_c})}$   
 $\parallel G \parallel$  plot showing magnitude response.


low Q approx:  $\omega_c = \frac{\omega_c}{Q}$





# Block Diagrams

Rules:

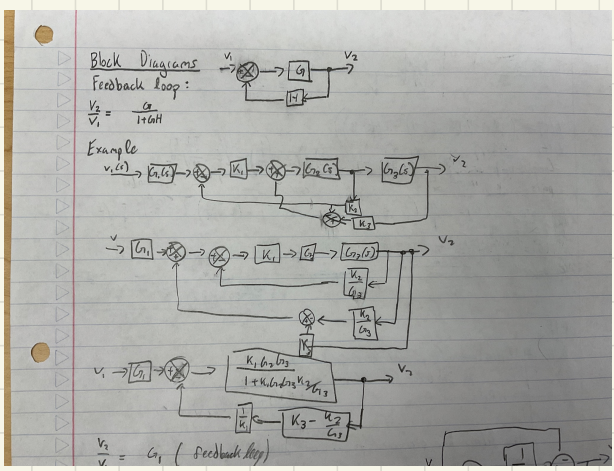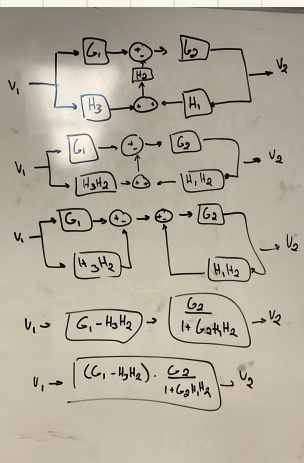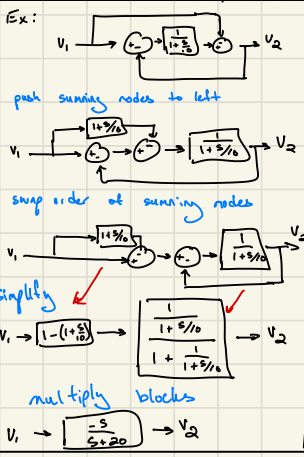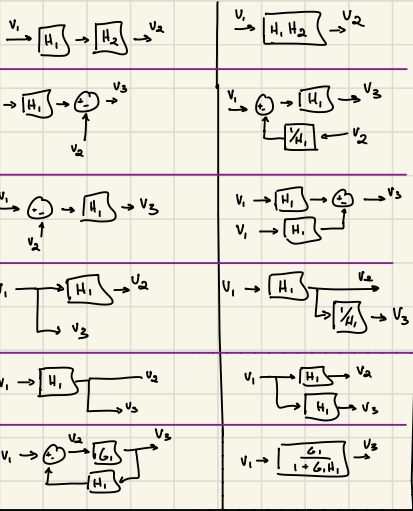

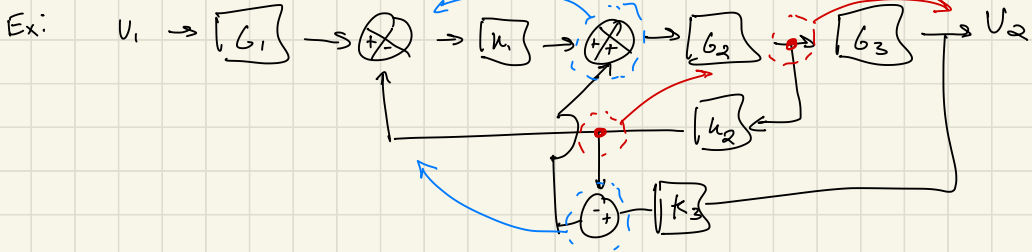


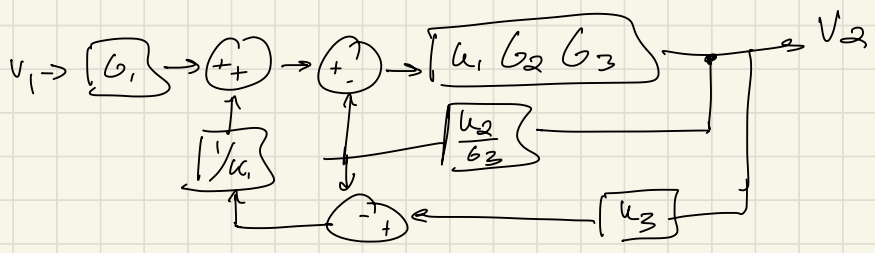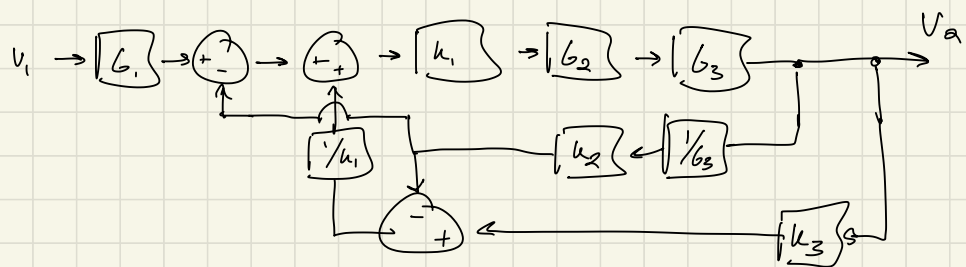pickoff points to right side  
 summing nodes to left side



$$v_1 \rightarrow \left[ \frac{k_1 G_1 G_2 G_3}{1 + k_1 k_2 G_2 + G_2 k_2 - G_2 G_3 k_3} \right] \rightarrow v_2$$
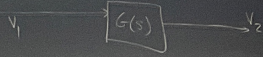
$$v_1(t) = a_0 + \sum_{n=1}^{\infty} A_n \cos(\omega_n t + \theta_n)$$



$$v_2(t) = v_0 + \sum_{n=1}^{\infty} V_n \cos(\omega_n t + \varphi_n)$$

$$v_0 = a_0 \cdot G(0)$$

$$V_n = A_n \|G(j\omega)\|, \quad \varphi_n = \theta_n + \angle G(j\omega)$$

$$V_2 = A_2 \cdot \|G(j2\omega)\|, \quad \varphi_2 = \theta_2 + \angle G(j2\omega)$$

$$V_n = A_n \|G(jn\omega)\|, \quad \varphi_n = \theta_n + \angle G(jn\omega)$$

$$v_2(t) = a_0 \cdot G(0) + \sum_{n=1}^{\infty} A_n \|G(jn\omega)\| \cos(\omega_n t + \theta_n + \angle G(jn\omega))$$



# Second Order Systems

$$G(s) = \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2} = \frac{1}{1 + 2\zeta \frac{s}{\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

$$\frac{1}{Q} = 2\zeta$$

$Q > \frac{1}{2} \equiv \zeta < 1$

complex poles

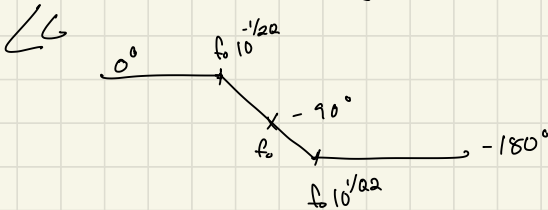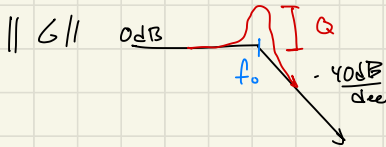

$Q < \frac{1}{2} \equiv \zeta > 1$

2 Real Poles



$G(s)$  will factor to

$$\frac{1}{\left(1 + \frac{s}{\omega_1}\right)\left(1 + \frac{s}{\omega_2}\right)}$$

low  $Q$  approx:

$$\omega_1 \approx Q\omega_0$$

$$\omega_2 \approx \frac{\omega_0}{Q}$$

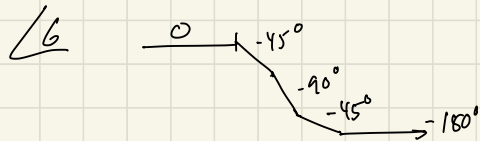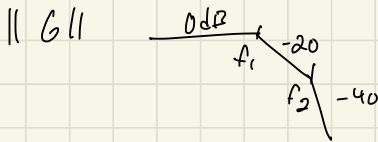

# Forms of Fourier Series

Rectangular :



$$v(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos(n\omega t) + b_n \sin(n\omega t)$$

Polar :

$$v(t) = a_0 + \sum_{n=1}^{\infty} A_n \cos(n\omega t + \theta_n)$$

Complex :
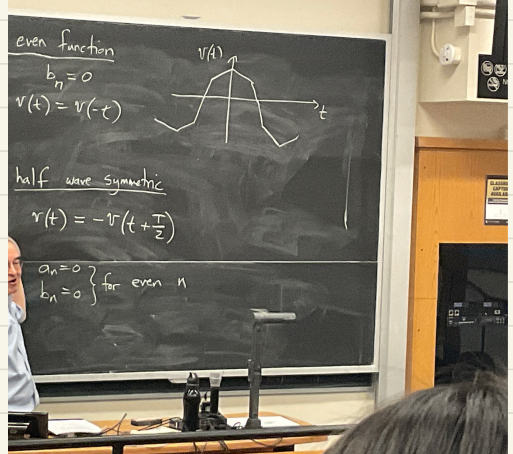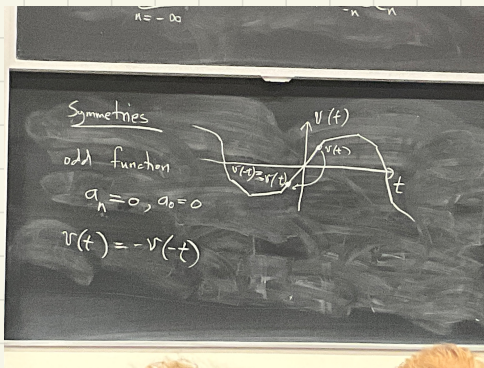
$$v(t) = \sum_{n=-\infty}^{\infty} C_n e^{jn\omega t} \quad \text{where } C_{-n} = C_n^*$$



# Final Exam 1

①

a)

$$F(s) = \frac{2s}{(s+2)(s^2+4s+5)}$$


$s = -2$

$$\frac{-4 \pm \sqrt{16 - 20}}{2}$$

$$\frac{-4 \pm 2i}{2}$$

$$= -2 \pm i$$

$A + B$

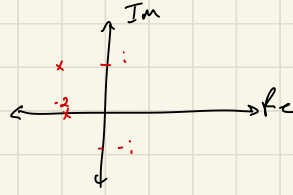

partial fraction

$$F(s) = \frac{k_1}{s+2} + \frac{k_2}{s-(-2+i)} + \frac{k_3}{s-(-2-i)}$$

$$k_1 = (s+2)F(s) \Big|_{s \rightarrow -2} = \frac{2s}{s^2+4s+5} = \frac{-4}{4-8+5} = \frac{-4}{1} = -4$$

$$k_2 = (s+2-i)F(s) \Big|_{s \rightarrow -2+i} = \frac{2s}{(s+2)(s-(-2-i))} = \frac{2(-2+i)}{(-2+i+2)(-2+i+2+i)} = \frac{-4+2i}{i(2i)}$$

$$\frac{-4+2i}{-2} = \frac{-4+2i}{-2} = 2-i$$

$$F(s) = \frac{-4}{s+2} + \frac{2-i}{s-(-2+i)}$$

$$\|k_2\| = \sqrt{4+1} = \sqrt{5}$$


$\left. \begin{matrix} \int \int \\ \downarrow \end{matrix} \right\}$

$$f(t) = -4e^{-2t} + 2\sqrt{5}e^{-2t} \cos\left(t - \frac{\pi}{4}\right)$$

$$\angle k_2 = \tan^{-1}\left(\frac{-1}{2}\right) = -45^\circ$$

$$F(s) = \frac{2s}{(s^2+4)(s+2)}$$

roots:  $-2, \pm 2$

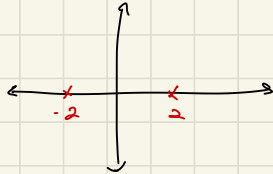

$$F(s) = \frac{2s}{(s+2)^2(s-2)}$$

$$\frac{1}{(s+2)^2} = \frac{2s}{(s+2)(s-2)}$$

$$F(s) = \frac{1}{s+2} \cdot \frac{k_1}{(s+2)} + \frac{k_2}{(s-2)}$$

$$k_1 = \frac{2s}{(s-2)} \Big|_{s \rightarrow -2} = \frac{-4}{-4} = 1$$

$$k_2 = \frac{2s}{s-2} \Big|_{s \rightarrow 2} = \frac{4}{0} = \infty$$

$$F(s) = \frac{1}{s+2} \left( \frac{1}{s+2} + \frac{1}{s-2} \right)$$

$$\frac{1}{(s+2)^2} + \frac{1}{(s+2)(s-2)}$$

$$\frac{1}{(s+2)^2} + \frac{1}{4(s-2)} - \frac{1}{4(s+2)}$$

$$\frac{k_1}{s+2} + \frac{k_2}{s-2}$$

$$k_1 = \frac{1}{(s+2)} \Big|_{s \rightarrow -2} = -\frac{1}{4}$$

$$k_2 = \frac{1}{s+2} \Big|_{s \rightarrow 2} = \frac{1}{4}$$

$$\Rightarrow f(t) = -\frac{1}{4}e^{-2t} + \frac{1}{4}e^{-2t} \cos\left(t - \frac{\pi}{4}\right) - \frac{1}{4}e^{-2t}$$

$$2) v(t) = (2(t+2)) \cdot (u(t+1) - u(t-3))$$

Laplace

a) period = 4

$$v(t) = 2(t+2)u(t+1) - 2(t-2)u(t-3)$$

$$\int v(t) = 2(t+1-1) - 2(t-3+1) \\ (2(t+1)-2)u(t+1) - (2(t-3)+2)u(t-3)$$

$$\frac{2e^{-s}}{s^2} \cdot \frac{2e^{-s}}{s} - \frac{2e^{-3s}}{s^2} + \frac{2e^{-3s}}{s}$$



$$v(t) = \frac{2e^{-s}}{s^2} \cdot \frac{2e^{-s}}{s} - \frac{2e^{-3s}}{s^2} + \frac{2e^{-3s}}{s} \\ \hline 1 - e^{-4s}$$

b)  $C_n = \frac{1}{T} v_1(j\omega n) \quad s = j\omega n \quad ???$

$$v_1(s) = \frac{2}{s} e^{-s} \left( \frac{1}{s} - 1 - \frac{1}{s} e^{-2s} - e^{-2s} \right) \\ \frac{2}{j\omega n T} e^{-j\omega n} \left( \frac{1}{j\omega n} - 1 - \frac{e^{-2j\omega n}}{j\omega n} - e^{-2j\omega n} \right)$$

c)  $v(t) = \sum_{n=1}^{\infty} (a_n \cos(n\omega t)) + b_n (\sin(j\omega t))$

$$v(t) = \sum_{n=1}^{\infty} b_n$$

$b_n = j C_n$  ↗

③  $V_{in} \rightarrow \boxed{G(s)} \rightarrow V_{out}$

second order  
high pass

$f_c = 5 \text{ kHz}$


critically damped

20 dB @ high freq

$$G(s) = \frac{G_0 \checkmark = 10 \rightarrow 20 \text{ dB}}{1 + \frac{\omega_0}{sQ} + \frac{\omega_0^2}{s^2}}$$

$\omega_0 = \frac{5000}{2\pi}$

④

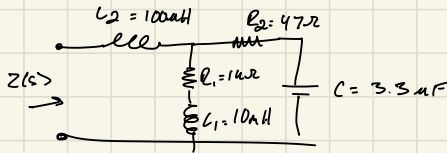

$$L_2 + (R_2 \parallel C) \parallel (R_1 \parallel L_1)$$

$$L_2 s + \frac{1}{\frac{1}{R_2} + sC} \parallel \frac{1}{\frac{1}{R_1} + \frac{1}{L_1 s}}$$

$$L_2 s + \frac{R_2}{1 + sCR_2} \parallel \frac{R_1 L_1 s}{L_1 s + R_1}$$

$$L_2 s + \frac{1}{\frac{1 + sCR_2}{R_2} + \frac{L_1 s + R_1}{R_1 L_1 s}}$$

$$L_2 s + \frac{R_2 R_1 L_1 s}{(R_1 L_1 s)(1 + sCR_2) + (L_1 s + R_1)R_2}$$




$$C_2 + (R_1 + L_1) \parallel (R_2 + C)$$

$$R_2 = 47\Omega = 33\text{dB}$$

$$R_1 = 1\text{k}\Omega = 60\text{dB}$$

Good

6 cycle semilog axes

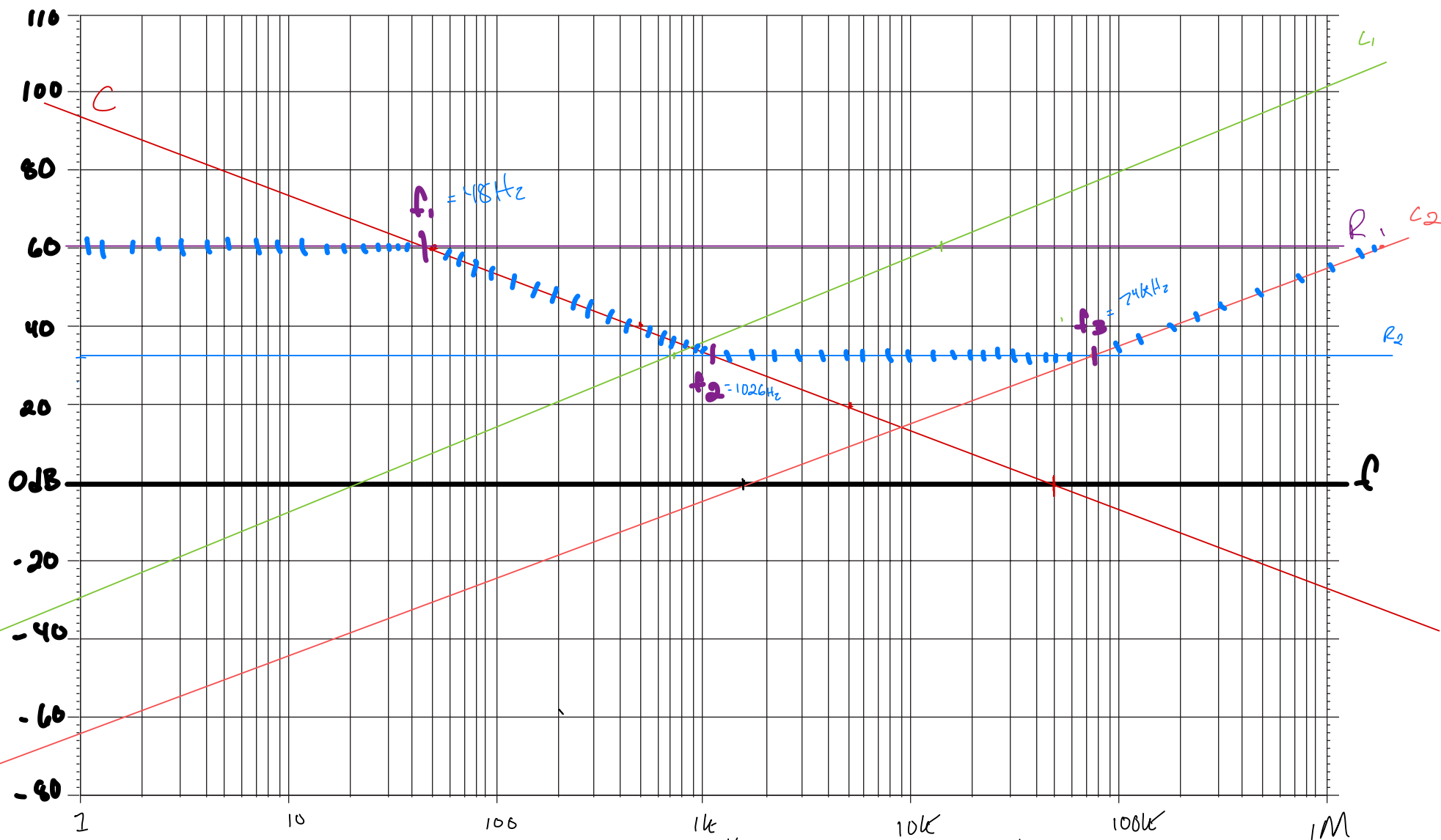

C crosses axis @  $\frac{1}{2\pi \cdot 3.3 \times 10^6} = 48.208\text{kHz}$

R2 crosses C @  $\frac{1}{2\pi R_2 C} = 1026\text{ Hz} = f_1$

L2 crosses R1 @  $\frac{1\text{k}}{2\pi \cdot 100 \times 10^6} = 1.5\text{ MHz}$

$\hookrightarrow R_2 = 74\text{ kHz}$

axis @  $\frac{1}{2\pi} = 1.6\text{ Hz}$

L1 crosses R1 @  $\frac{1\text{k}}{2\pi \cdot 10 \times 10^7} = 15915 \text{ or } 15\text{ kHz}$

$\hookrightarrow R_2 @ 748\text{ Hz}$

$$\textcircled{5} \quad G(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{R_2 + \frac{1}{sC}}{(R_2 + \frac{1}{sC}) + (Ls + R_1)} = \frac{R_2 sC + 1}{(R_2 sC + 1) + sC(Ls + R_1)} = \frac{R_2 sC + 1}{R_2 sC + 1 + s^2 CL + R_1 sC} = \frac{R_2 sC + 1}{(R_1 + R_2) sC + s^2 CL + 1}$$

$$\text{zero: } R_2 sC + 1 = \frac{1}{R_2 C 2\pi} \quad \cdot \quad 3 \text{ kHz} = f_c$$

$$\text{pole: } (R_1 + R_2) sC + s^2 CL + 1$$

$$s^2 CL = \left(\frac{s}{\omega_0}\right)^2 = CL = \frac{1}{\omega_0^2} \quad \omega_0 = \sqrt{\frac{1}{CL}}$$

$$3162 \text{ Hz} = \omega_0$$


$$f_0 = 503 \text{ Hz}$$

$$\frac{1}{Q(3.16 \text{ kHz})} = (R_1 + R_2) C$$

$$Q = \frac{1}{(R_1 + R_2) C (3.16 \text{ kHz})}$$


$$Q = 2.06$$

6 cycle semilog axes






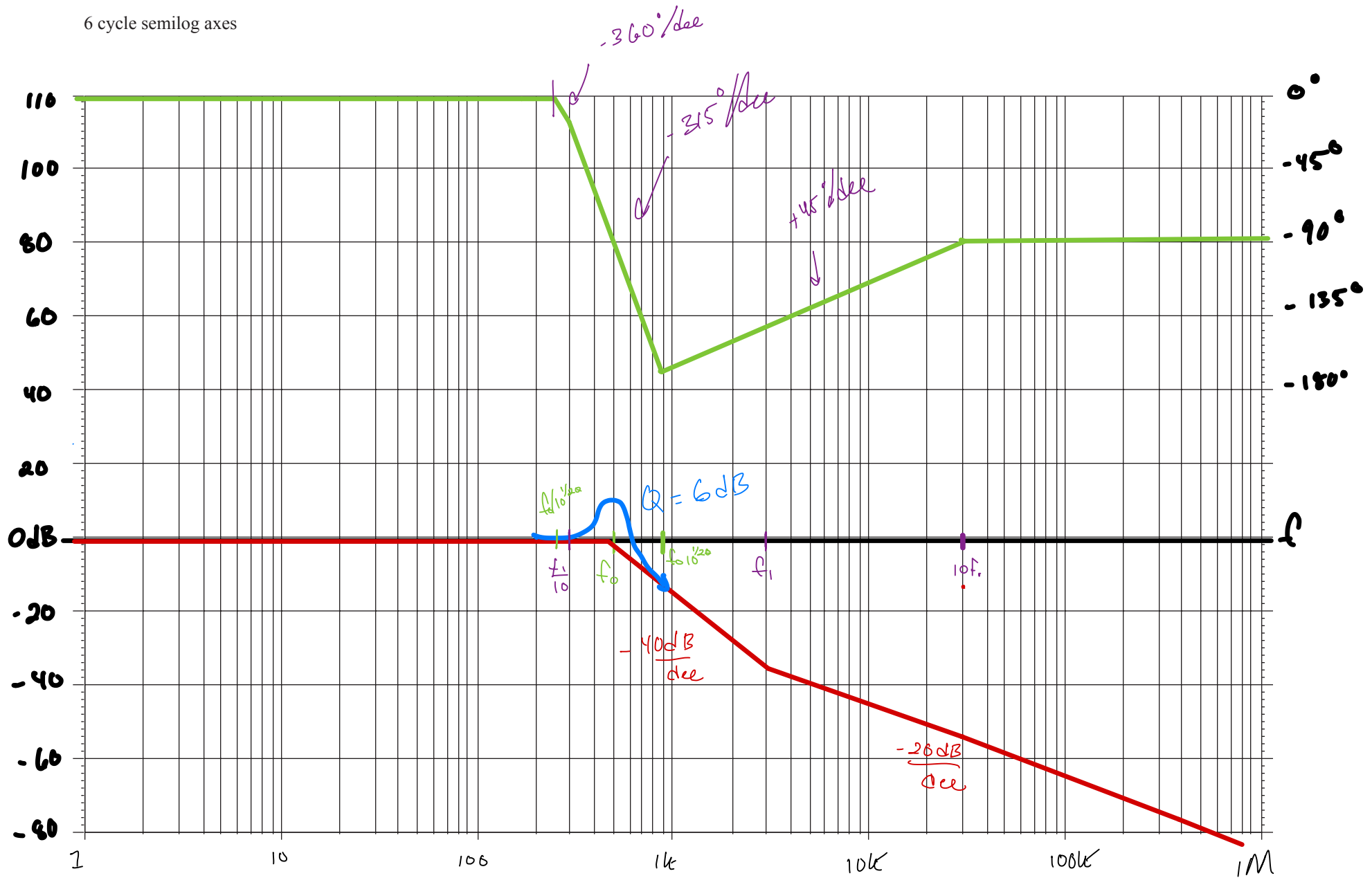


$\frac{f}{10^{1/20}} = 281$ 
 $f_0 \cdot 10^{1/20}$

6

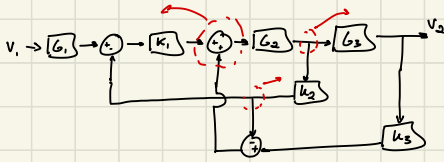

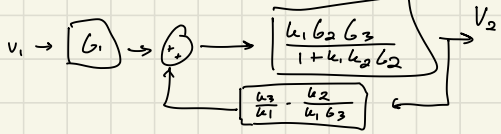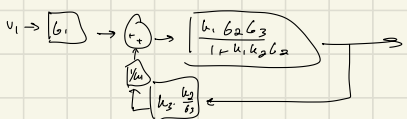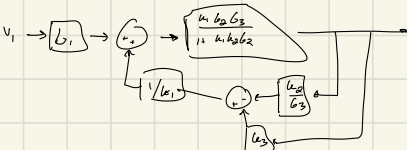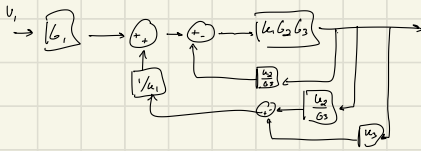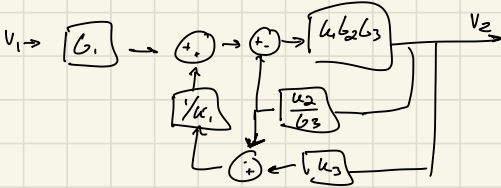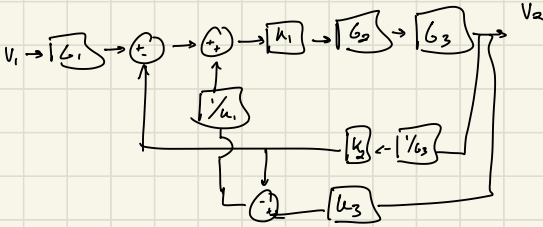
push nodes to left  
push points to right



$$\frac{V_1}{V_2} = G_1 \cdot \frac{k_1 G_2 G_3}{1 + k_1 k_2 G_2} \left( 1 + \left( \frac{k_1 G_2 G_3}{1 + k_1 k_2 G_2} \right) \left( \frac{k_2 G_2 k_3}{G_2 G_3 k_1} \right) \right)$$

$$G_1 \cdot \frac{k_1 G_2 G_3}{1 + k_1 k_2 G_2} \left( 1 + \frac{G_2 \cdot (k_2 \cdot G_3 \cdot k_3)}{1 + k_1 k_2 G_2} \right)$$

force node to be negative

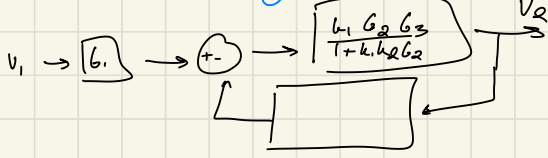

a) even

$$4 \int_0^{T/2} v(t) \cos(n\omega t) dt$$

$$A_n = a_n$$

$$\theta_n = \tan^{-1} \left( \frac{0}{a_n} \right)$$

$$= 0$$

b) odd symmetry  $a_0 = 0$   
 $a_n = 0$   
 $b_n = \frac{4}{T} \int_0^{T/2} v(t) \sin(n\omega t) dt$

$$\frac{4}{T} \int_0^{T/2} \frac{I_{pk} \cdot T}{2} \sin(n\omega t) dt$$

$$A_n = b_n \quad \theta_n = \tan^{-1} \left( \frac{b_n}{0} \right) = \pi/4$$

c) even half wave

② a) Fourier Series of function  
 $T = 2\pi$  even half wave

$$\left. \begin{array}{l} a_n = 0 \\ b_n = 0 \end{array} \right\} \text{ for } n = 0, 2, 4$$

$$a_n = \begin{cases} 0, & \text{even } n \\ \frac{4}{\pi} \int_0^{\pi/2} V(t) \cos(n\omega t) dt, & \text{odd } n \end{cases}$$

$$b_n = 0$$

$$a_n = \frac{4}{2\pi} \int_0^{\pi}$$